

## Rectification

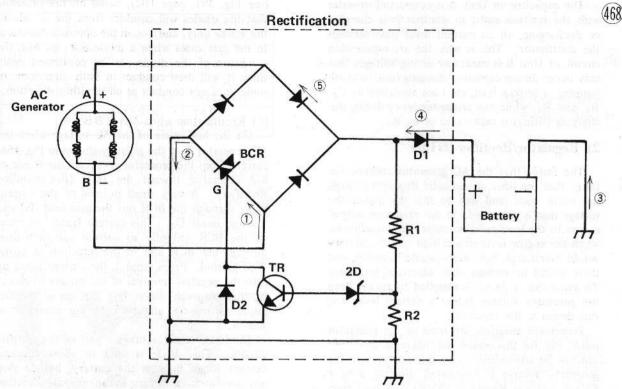

## Rectification

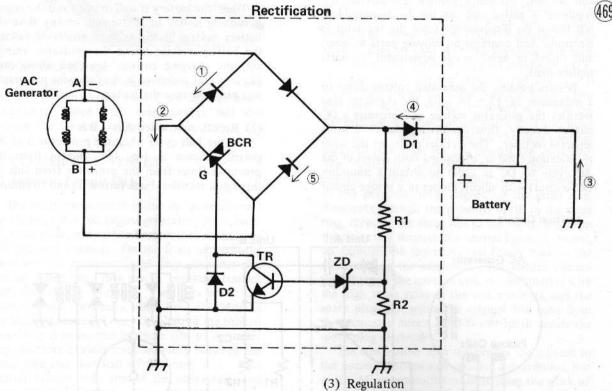

From ground, the current flows up into the negative side of the battery to charge it, through diode  $D_1$  and the rectifier diode (arrow 5), and back into the generator on side B.

In either of the cases of rectification explained above, there is also another path for current in the regulator, and this is through R<sub>2</sub> and R<sub>1</sub>. This is a very small current, but it serves to always keep a representative portion of the generator voltage at the cathode of the Zener diode (ZD).